

Application Note 1321

Industrial Field Bus Networks

Before field bus, an industrial control system was built up around a central controller with input and output cards to input signals from sensors and output signals to actuators. Usually, the controller, I/O cards and motor drivers were installed in the central cabinet, which was connected with the remote devices (Figure 1a).

Field bus networks, however, communicate between the controller and field devices in a sequential information manner (Figure 1b). Controllers and devices are connected to the field bus cable in bus, star, tree or ring topologies.

From the mid 1980's, field bus technology was ready to move onto the factory floor. Industrial field buses are classified according to their performance capabilities. What field bus standard one ultimately chooses chiefly depends upon the amount of data that a bus is able to handle and its associated speed or propagation delay requirements. There are perhaps dozens of popular network standards and hundreds of proprietary or home brewed standards. The development and usage of field buses has grown rapidly. During the end of 1999 and 2000, there was approval for IEC61158, which is an international standard covering several networks in total. Appendix 1 lists a performance comparison of some popular field bus standards discussed in this application note.

Optical Isolation for Field Bus Networks

Numerous and large transient bursts are common in an industrial environment. These transient bursts can disrupt the data transmission and even potentially damage the interconnected equipment. In order to ensure error-free data transmission in high-speed field bus communication, an industry system designer has to take efforts to eliminate disturbances. Typically galvanic isolated optocouplers (Figure 2) are used to retain data integrity and protect interconnected equipment.

International standard IEC 61000-4-4 specifies electrical fast transient/burst immunity test related to the immunity requirement of EMC. All of Avago Technologies' high-speed CMOS optocouplers have transient immunity performance CMR 10 kV/ μ s at common mode voltage up to 1000 Volts. Optocouplers isolate transient/burst interference and transmit data between bus transceiver and controller. Since network communication is bi-directional (involving receiving data from and transmitting data onto the network) two optocouplers are needed per node.

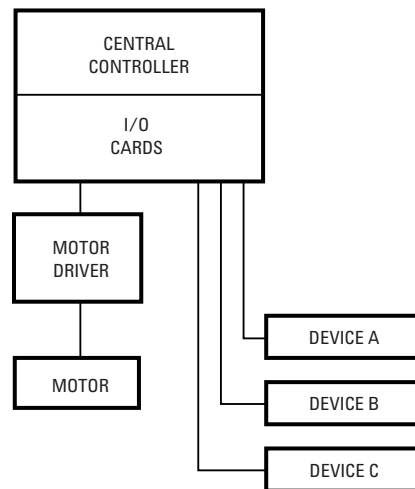


Figure 1a. Conventional controller and remote devices connected by parallel

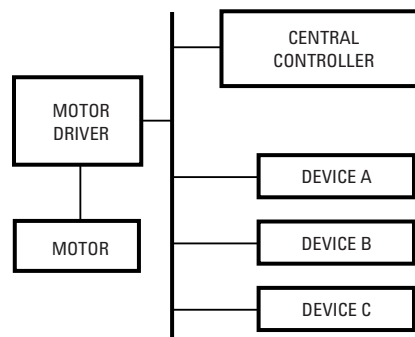


Figure 1b. Controller and remote devices connected by fieldbus network

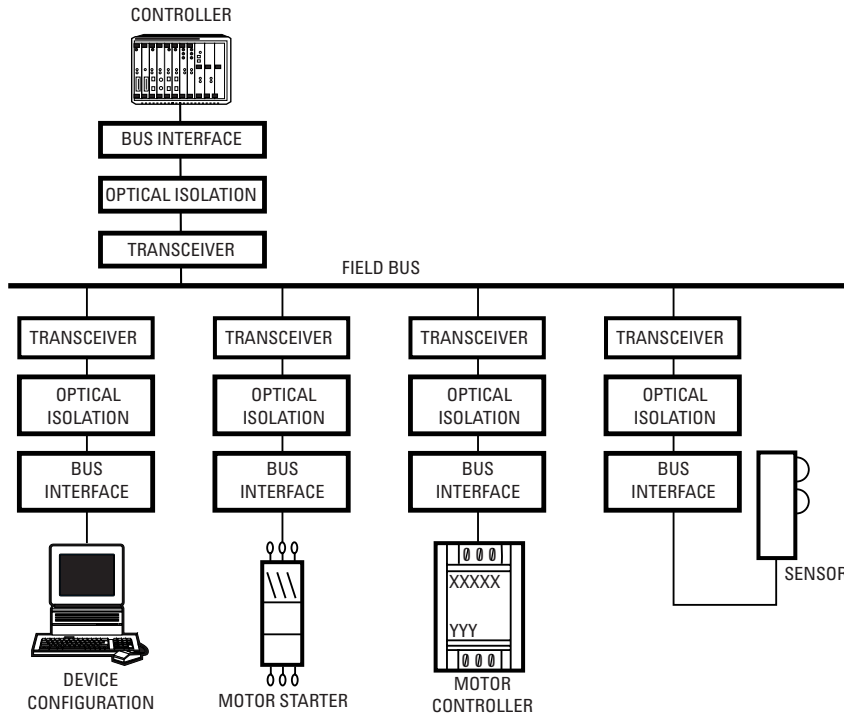


Figure 2. Field Bus Communication Physical Model

Recommended Optocouplers

The following optocouplers use the latest CMOS IC technology to achieve outstanding system performance. The optocoupler choice will depend on the overall system requirements, with data rate and regulatory requirements playing an important role.

HCPL-	7710	0710	7720	0720	7721	0721	0708	0738	7723	0723
Speed	12.5 MBd		25 MBd				15 MBd		50 MBd	
Max. Propagation Delay	40 ns						60 ns		22 ns	
Min. Pulse Width	80 ns		40 ns				100 ns		20 ns	
Max. PWD	8 ns				6 ns		30 ns		2 ns	
Max. Propagation Delay Skew	20 ns						40 ns		15 ns	
Min. CMR	10 kV / μ s @ $V_{cm} = 1000$ V									
Package Type	300 mil DIP8	SO8	300 mil DIP8	SO8	300 mil DIP8	SO8	SO8	SO8 Dual	300 mil DIP8	SO8
IEC/EN/DIN EN 60747-5-2 [Viorm]	*630 Vpeak	*560 Vpeak	*630 Vpeak	*560 Vpeak	*630 Vpeak	*560 Vpeak	*560 Vpeak		*630 Vpeak	*560 Vpeak
UL [Viso]	3750 Vrms	3750 Vrms	3750 Vrms	3750 Vrms	3750 Vrms	3750 Vrms	3750Vrms		3750 Vrms	3750 Vrms

* Option 060 required.

Isolation Node Power Supply

Design Considerations

There are an AC line in device power supplies and DC power in field bus cables. It is very flexible for the isolation node to tap power from the above two sources. The basic consideration is that two power supplies must be isolated across the optocoupler isolation boundary. There are three types of solutions, namely:

1. Isolation Node Powered by the Network (Figure 3);
2. Isolation Node with Transceiver Powered by the Network (Figure 4);
3. Isolation Node Providing Power to the Network (Figure 5).

1. Isolation Node Powered by the Network

If the network power can supply the devices sufficiently, then it is not necessary to power field devices from the AC line. As seen in Figure 3, a non-isolated voltage regulator supplies the transceiver and half of two optocouplers, while an isolated DC/DC converter supplies the controller and the other side of two optocouplers.

2. Isolation Node with Transceiver Powered by the Network

Figure 4 shows when an application requires a significant amount of power. In this case, the field device is powered by the AC line source while the transceiver and isolated side of the two optocouplers are powered by the network. This method is also desirable as it does not heavily load the network.

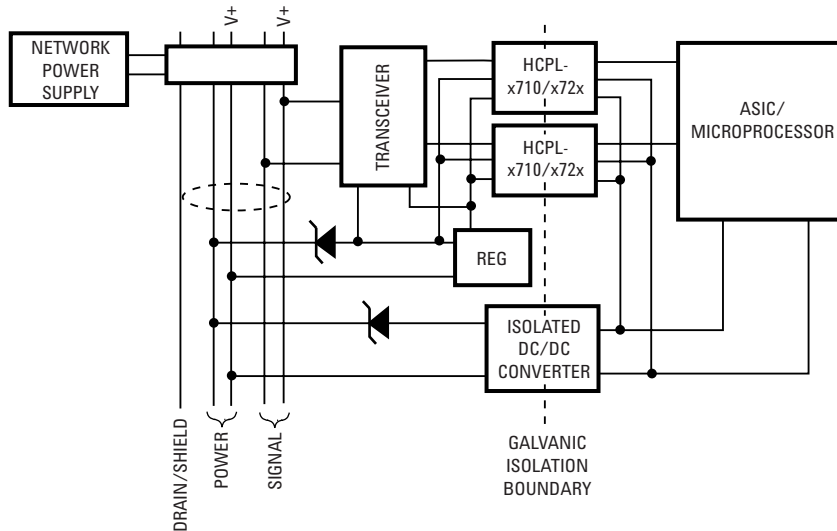


Figure 3. Isolation Node Powered by the Network

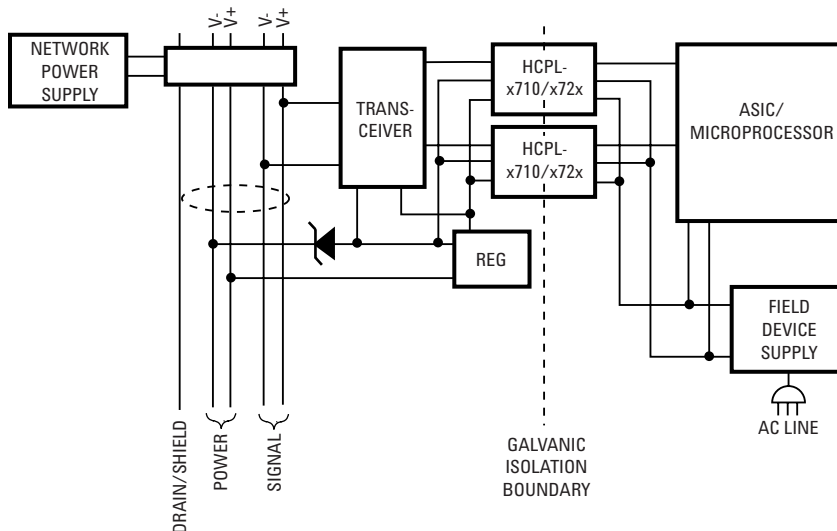


Figure 4. Isolation Node with Transceiver Powered by the Network

3. Isolation Node Providing Power to the Network

The method shown in Figure 5 is recommended when there are a limited number of devices on the network that do not require much power, thus eliminating the need for separate network power supplies. The AC line powers the field device supply locally and also powers the isolated power supply. This supply powers the network, from which one regulator derives DC 5 V to power the transceiver and the isolated (network) side of two optocouplers.

Recommended DeviceNet Application Circuit

A CAN bus is used by DeviceNet physical layer implementation. The recommended DeviceNet application circuit is shown in Figure 6. Since the high-speed CMOS optocouplers HCPL-x710/x72x are fully compatible with CMOS logic level signals, the two optocouplers are connected directly to the CAN transceiver. Two bypass capacitors (with values between 0.01 and 0.1 μF) are required and should be located as close as possible to the input and output power supply pins of the optocoupler. For each capacitor, the total lead length between both ends of the capacitor and the power supply pins should not exceed 20 mm. The bypass capacitors are required because of the high-speed digital nature of the signals inside the optocoupler.

More importantly, the unique “dual-inverting” design of the Avago Technologies' HCPL-x710/x72x ensures the network will not “lock-up” if either AC line power to the node is lost or the node powered-off. Specifically, when input power (V_{DD1}) to the HCPL-x710/x72x located in the transmit path is eliminated, a RECESSIVE bus state is ensured as the HCPL-x710/x72x output voltage (V_O) goes HIGH.

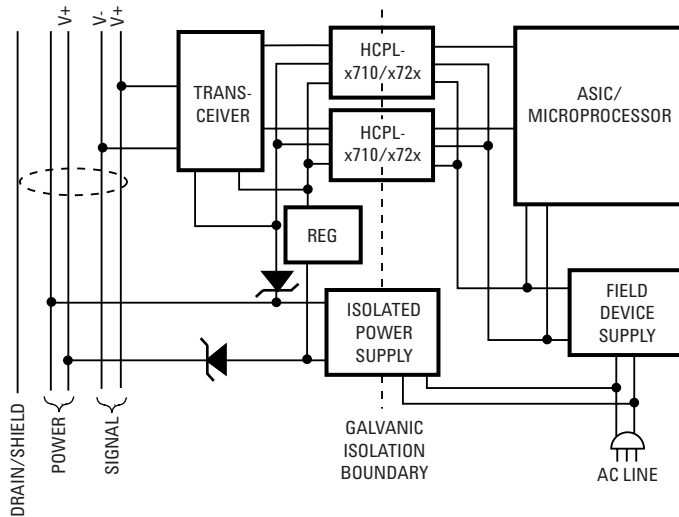


Figure 5. Isolation Node Providing Power to the Network

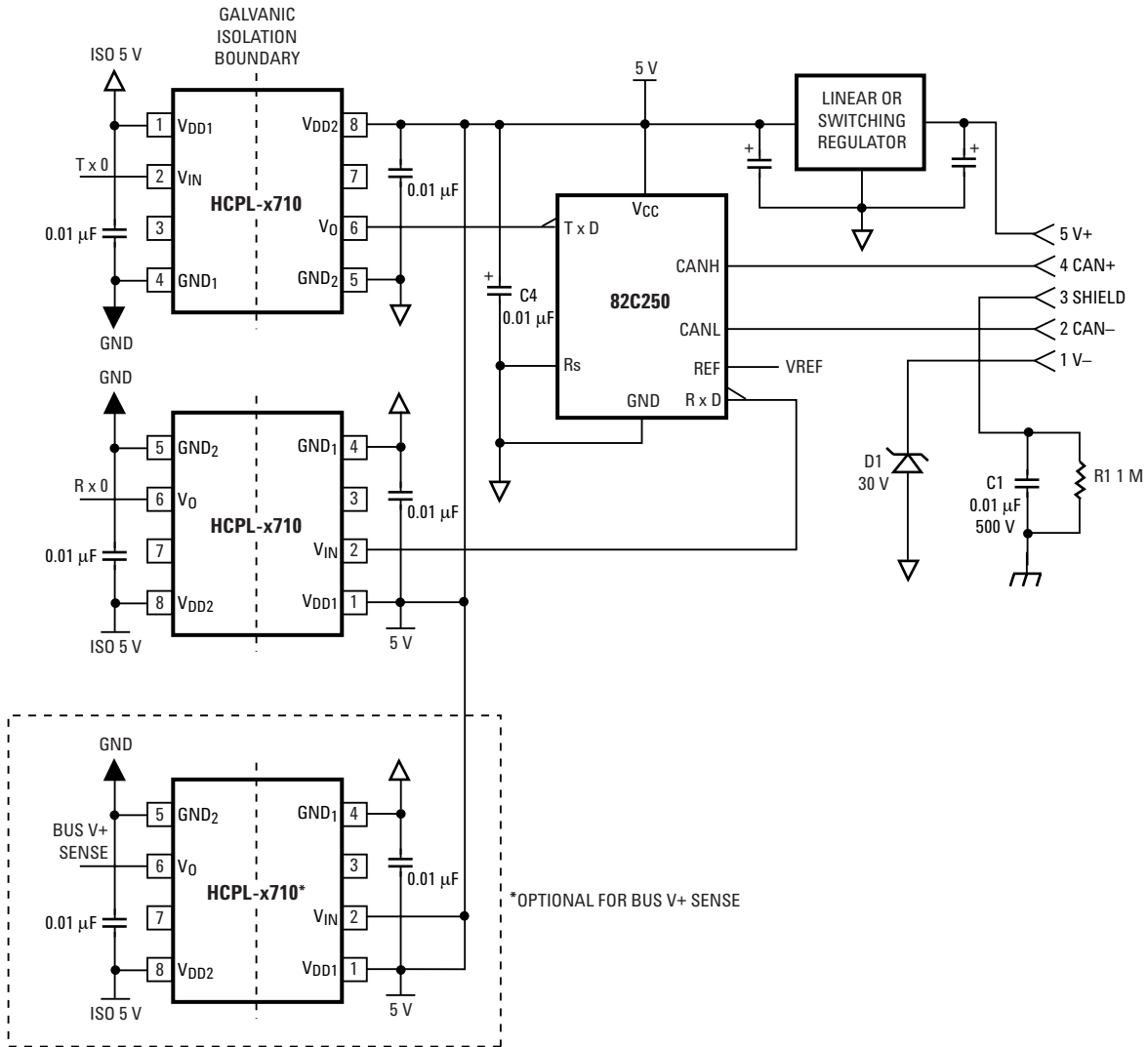


Figure 6. Recommended DeviceNet Application Circuit

***Bus V+ Sensing**

It is suggested that the Bus V+ sense block shown in Figure 6 be implemented. A locally powered node with an unpowered isolated Physical Layer will accumulate errors and become bus-off if it attempts to transmit. The Bus V+ sense signal would be used to change the BOI attribute of the DeviceNet Object to the "auto-reset" (01) value. Refer to DeviceNet Specification Volume 1, Section 5.5.3. This would cause the node to continually reset until bus power was detected. Once power was detected, the BOI attribute would be returned to the "hold in bus-off" (00) value. The BOI attribute should not be left in the "auto-reset" (01) value since this defeats the jabber protection capability of the CAN error confinement.

Recommended PROFIBUS Application Circuit

In PROFIBUS physical layer implementation, transmission technologies RS485 and IEC1158-2 are adopted by PROFIBUS. The recommended PROFIBUS application circuit is shown in Figure 7. Since the high-speed CMOS optocouplers HCPL-772x/072x are fully compatible with CMOS logic level signals, the optocouplers are connected directly to the transceiver. Two bypass capacitors (with values between 0.01 and 0.1 μF) are required and should be located as close as possible to the input and output power-supply pins of the optocoupler. For each capacitor, the total lead length between both ends of the capacitor and the power supply pins should not exceed 20 mm. The bypass capacitors are required because of the high-speed digital nature of the signals inside the optocoupler.

Being very similar to multi-station RS485 systems, the HCPL-061N optocoupler provides a transmit disable function which is necessary to make the bus free after each master/slave transmission cycle. Specifically, the HCPL-061N disables the transmitter of the line driver by putting it into a high state mode. In addition, the HCPL-061N switches the RX/TX driver IC into the listen mode. The HCPL-061N offers HCMOS compatibility and the high CMR performance (1 kV / μs at $V_{\text{CM}} = 1000 \text{ V}$) essential in industrial communication interfaces.

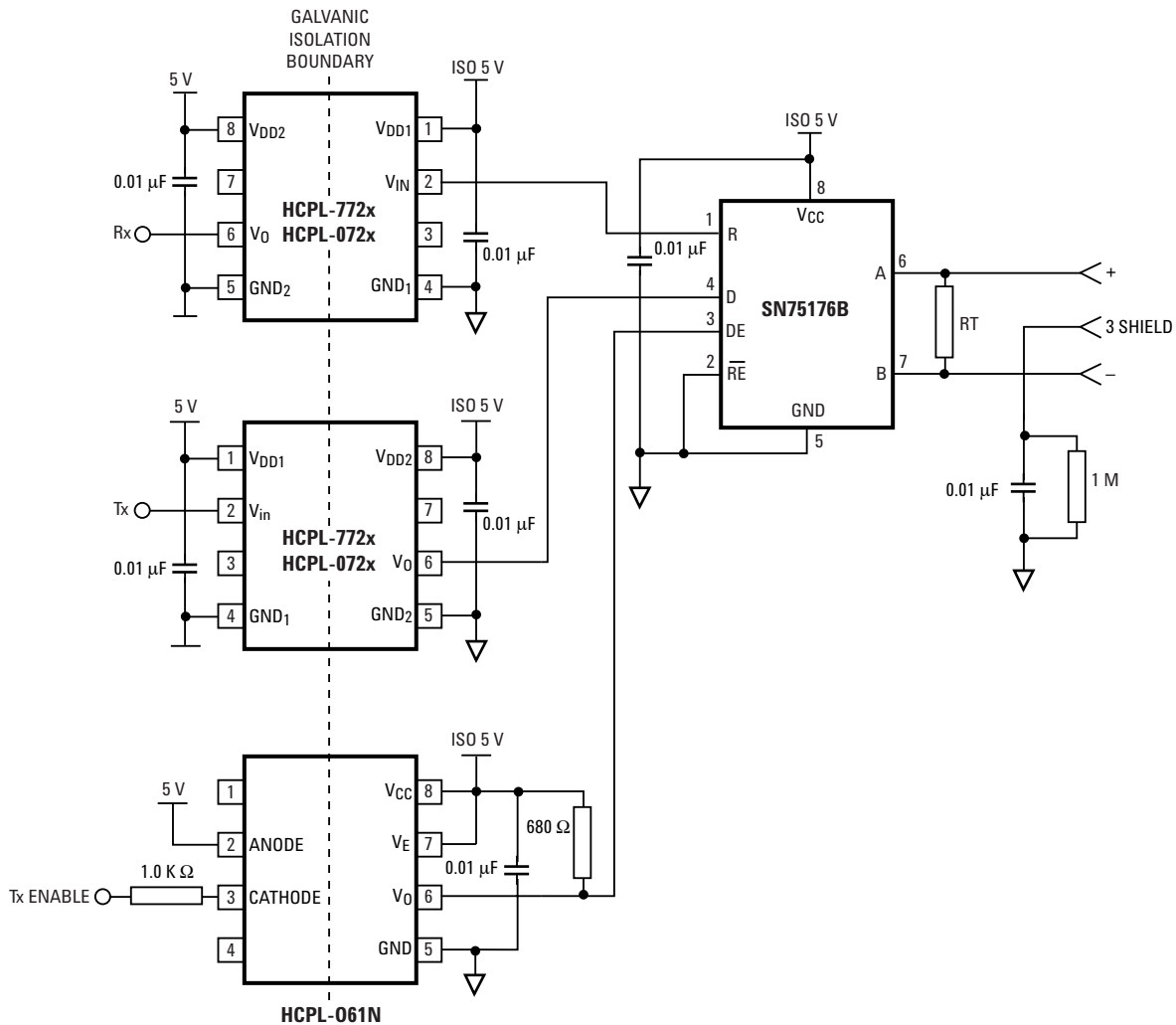


Figure 7. Recommended PROFIBUS Application Circuit

Recommended CC-Link Application Circuit

CC-Link (Control and Communication Link) is developed to merge control and information in the low-level network (field network) by PCs, thereby making the multivendor environment a reality. It has data control and message-exchange function, as well as bit control function, and operates at the speed up to 10 Mbps.

The recommended CC-Link circuit is shown in Figure 8. Since the Avago Technologies HCPL-772x/072x are fully compatible with CMOS logic level signals, the optocouplers are connected directly to the transceiver. Two bypass capacitors (with values between 0.01 μF

and 0.1 μF) are required and should be located as close as possible to the input and output power supply pins of the HCPL-772x/072x. For each capacitor, the total lead length between both ends of the capacitor and power supply pins should not exceed 20 mm. The bypass capacitors are required because of the high-speed digital nature of the signals inside the optocoupler. Two HCMOS-compatible and low cost optocouplers HCPL-2611 transmit Enable signals to the receiver and driver separately. Alternatively one dual-channel optocoupler HCPL-4661 or HCPL-0738 can be applied here to save cost and PCB size.

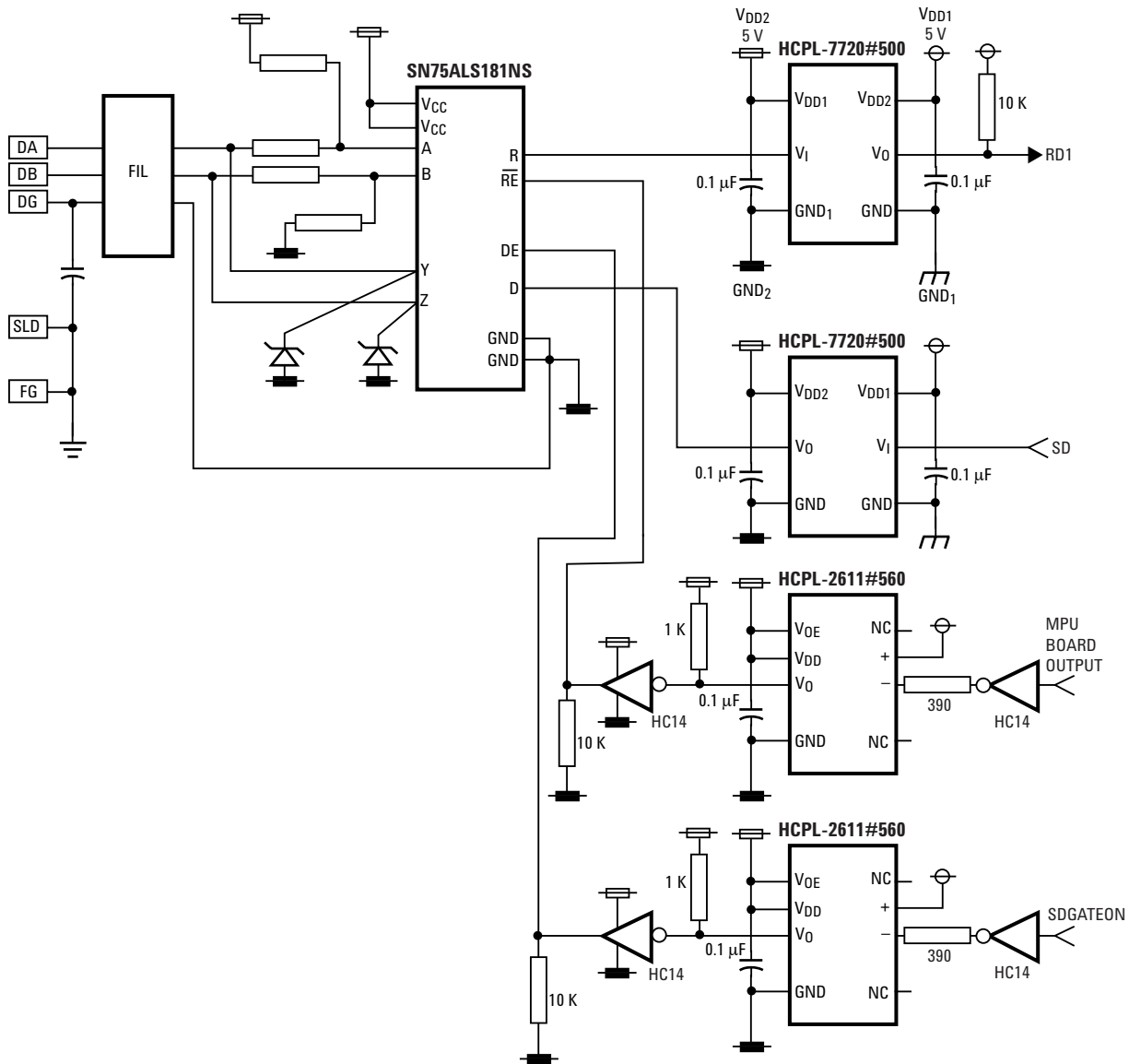


Figure 8. Recommended CC-Link Application Circuit

Appendix 1

Table 1. Popular Field Bus Specifications and Comparison

	CC-Link	DeviceNet	Profibus	CAN
Max. Devices or Nodes	64 per master	64	127 nodes (124 slaves -4 seg, 3 rptrs) + 3 masters	127
Max. Baud rate	156 Kbps to 10 Mbps depending upon distance	500 kBd	12 MBd (9.6 kBd to 12 MBd are supported)	1 Mbd
Max. Extension	1200 m (twisted pair), Master plus 10 repeaters = 13.2 Km	100 m at 500 kBd, 500m at 125 kBd, 6 km with repeaters	100 m between segments at 12 MBd, 24 km (Fiber) (baud rate and media dependent)	1 km at 10 kBd, 40 m at 1 MBd
Network Topology		Trunk line, drop line with branching	Line, Star, or Ring	Trunk line, drop line
Typical Applications	Commonly found in factory floor Processes	Most commonly found in assembly, welding, automotive, semiconductor, and material handling machines.	Commonly found in Process control and large assembly, and material handling machines	Commonly found in Automotive and Motion control systems, assembly, welding, and material handling machines
Technology Developer	Mitsubishi Electric	Layer 1, 2: Bosch AG, Layer 7: 1994 Rockwell Automation (Allen-Bradley)	Siemens Profibus DP (Decentral Periphery) 1994 Profibus PA (Process Automation) 1995	Layer 1, 2: Bosch AG, Layer 7: CAN In Automation, Philips, 1995

For product information and a complete list of distributors, please go to our web site: www.avagotech.com

Avago, Avago Technologies, and the A logo are trademarks of Avago Technologies, Pte. in the United States and other countries.

Data subject to change. Copyright © 2006 Avago Technologies Pte. All rights reserved.

5989-0340EN - May 23, 2006

